

**Assignment -1**  
Smart Street Light using Tinker CAD



Assignment Date	19 September 2022
Student Name	Mr. L. Dhinakar
Student Roll Number	611219106014
Maximum Marks	2 Marks

**Question-1:**

Make a Smart Street Light in Tinker CAD, using 2+ sensors, Led, Buzzer in single code and circuit.

Solution:

```
int LEDwhite = 10;
int DO_Sensor = 8;
int Sensitivity = 0;
//int relay = 7;
void setup() {
  pinMode(LEDwhite, OUTPUT);
  pinMode(DO_Sensor, INPUT);
  //pinMode(relay, OUTPUT);
}
void loop() {
  Sensitivity = digitalRead(DO_Sensor);
  if (Sensitivity == HIGH)
  {
    digitalWrite(LEDwhite, HIGH);
    //digitalWrite(relay, HIGH);
    delay(30000);
  } else {
    digitalWrite(LEDwhite, LOW);
    //digitalWrite(relay, LOW);
  }
}
```

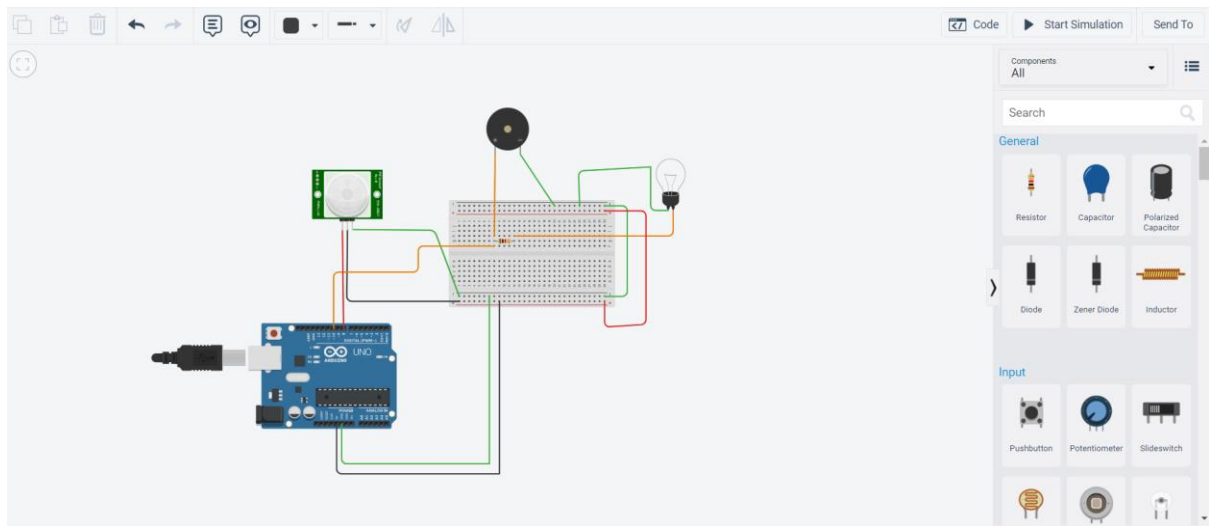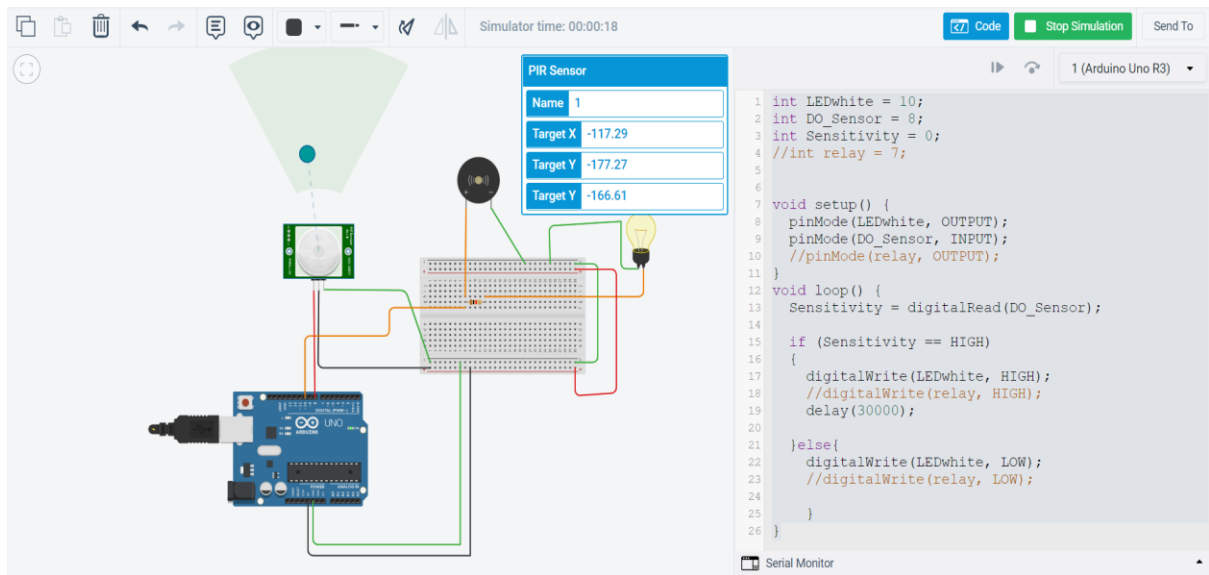

Link: <https://www.tinkercad.com/things/8eni9le8zs-j-assignment1/>