## Assignment -1 Home automation using Tinker CAD


Assignment Date	19 September 2022
Student Name	Mr. S. K. Srinivas Krishna
Student Roll Number	611219106073
Maximum Marks	2 Marks


## Question-1:

Make a Smart Home in Tinkercad, using 2+ sensors, Led, Buzzer in single code and circuit.
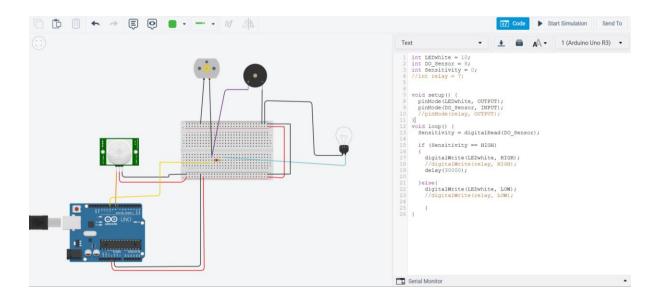
## Solution:

```
int LEDwhite = 10;
int DO_Sensor = 8;
int Sensitivity = 0;
void setup() {
pinMode(LEDwhite, OUTPUT);
pinMode(DO_Sensor, INPUT);
void loop() {
Sensitivity = digitalRead(DO_Sensor);
if (Sensitivity == HIGH)
{
digitalWrite(LEDwhite, HIGH);
delay(30000);
}else{
digitalWrite(LEDwhite, LOW);
}
}
```



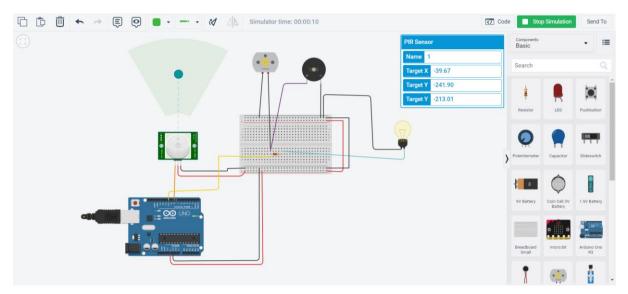

Link: https://www.tinkercad.com/things/fC4Qe1hVYzm-ibmassignment1/